

Lab 8: Simple SPI Transmitter

Ishabul Haque 111598085

Ken Ejinkonye 112011486

Section 2

04/10/20

```


1  -----
2  --
3  -- Title       : send_pos_edge_det
4  -- Design      : task1_2
5  -- Author      : Ishabul Haque and Ken Ejinkonye
6  -- Company     : Stony Brook
7  --
8  -- Description : A positive edge detector is used to detect the
9  -- positive edge of the send and to generate a narrow pulse that will
10 -- be used by the spi_tx_shifter to determine when it should start to send
11 -- a byte.
12 -- List of Circuit Features To Be Verified:
13 -- Inputs: rst_bar, clk, send
14 -- Outputs: send_en
15
16
17 -----
18
19 library IEEE;
20 use IEEE.std_logic_1164.all;
21
22 entity send_pos_edge_det is
23     port(
24         rst_bar : in std_logic;    -- asynynchronous system reset
25         clk : in std_logic;        -- system clock
26         send : in std_logic;       -- debounced send input
27         send_en : out std_logic    -- send enable output pulse
28     );
29 end send_pos_edge_det;
30
31
32 architecture moore_fsm of send_pos_edge_det is
33     type state is (state_a, state_b, state_c);
34     signal present_state, next_state : state;
35
36     begin
37         state_reg: process (clk,rst_bar)
38         begin
39             if rst_bar = '0' then
40                 -- If rst_bar is enabled, then present state will switch
41                 -- to state a
42                 present_state <= state_a;
43             elsif rising_edge(clk) then
44                 -- If rst_bar is not enabled, the present state will switch
45                 -- to the next state on the rising edge of clock
46                 present_state <= next_state;
47             end if;
48         end process;
49
50         outputs: process (present_state)
51         begin
52             case present_state is
53                 -- Output send_en will only be high when the present state
54                 -- is in state c, otherwise it will output low
55                 when state_c => send_en <= '1';

```

```
56         when others => send_en <= '0';
57     end case;
58 end process;
59
60     nxt_state: process (present_state, send)
61     begin
62         -- Moore FSM, state values are determined by
63         -- state diagram
64         case present_state is
65             when state_a =>
66                 if send = '0' then
67                     next_state <= state_b;
68                 else
69                     next_state <= state_b;
70                 end if;
71
72             when state_b =>
73                 if send = '1' then
74                     next_state <= state_c;
75                 else
76                     next_state <= state_b;
77                 end if;
78
79             when others =>
80                 if send = '0' then
81                     next_state <= state_b;
82                 else
83                     next_state <= state_a;
84                 end if;
85             end case;
86         end process;
87     end moore_fsm;
88
89
90
```

```
1  -----
2  ---
3  -- Title      : send_pos_edge_det_tb
4  -- Design     : task1_2
5  -- Author     : Ishabul Haque and Ken Ejinkonye
6  -- Company    : Stony Brook
7  --
8  -- Description : Non self checking testbench for send_pos_edge_det design.
9  --
10 -----
11 ---
12
13 library ieee;
14 use ieee.std_logic_1164.all;
15 use ieee.numeric_std.all;
16 library work;
17 use work.all;
18
19
20
21 entity send_pos_edge_det_TB is
22
23
24 end send_pos_edge_det_TB;
25
26 architecture tb_architecture of send_pos_edge_det_TB is
27
28     --stimulus signals
29     signal rst_bar : std_logic;
30     signal send : std_logic;
31     signal clk : std_logic;
32     --observed signals
33     signal send_en : std_logic;
34
35     constant period : time := 20ns; --need a much longer period
36                                     -- in actual hardware
37
38 begin
39     -- Unit Under Test port map
40     UUT: entity send_pos_edge_det
41     port map (
42         clk => clk,
43         rst_bar => rst_bar,
44         send => send,
45         send_en => send_en
46     );
47
48     rst_bar <= '0', '1' after period; -- reset
49
50     clock: process -- system clock
51     begin
52         -- clock starts at 0 for 0.5 clock periods
53         for i in 0 to 28 loop
54             wait for period;
55         end loop;
```

```
56         clk <= not clk;           -- 28 rising edges
57         wait for period;
58     end loop;                       -- stop clock
59     std.env.finish;
60 end process;
61
62 -- Duration of signal send is 200ns at a high value
63 snd: process
64 begin
65     for i in 0 to 28 loop          --28 rising edges
66         wait for 200ns;            -- Send pulse duration of 200ns
67         send <= not send;
68     end loop;                      --end pulse
69
70     std.env.finish;
71 end process;
72
73 end tb_architecture;
74
```

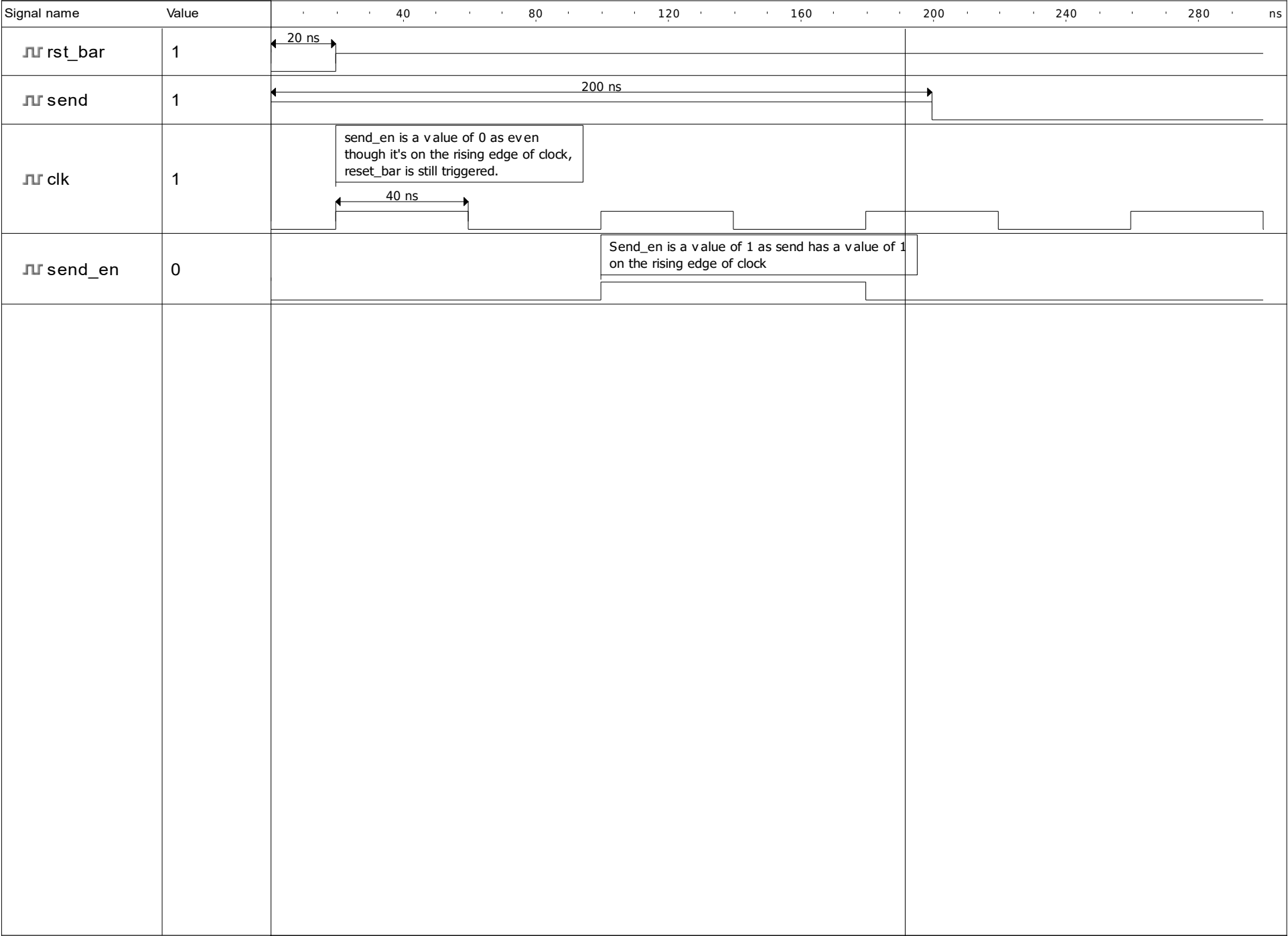

```

1  -----
2  --
3  -- Title      : spi_tx_shifter
4  -- Design     : task1_2
5  -- Author     : Ishabul Haque and Ken Ejinkonye
6  -- Company    : Stony Brook
7  --
8  -- Description : The transmitter shifter spi_tx_shifter converts the
9  parallel
10 -- data byte data_in to serial and transmits its data bits along with a
11 -- synchronous clock sck. An SPI slave uses sck to determine when to
12 -- sample
13 -- each serial data bit. We will be transmitting the data's most
14 -- significant
15 -- bit.
16
17 -- List of Circuit Features To Be Verified:
18 -- Inputs: rst_bar, clk, send_en, cpha, cpol, data_in
19 -- Inputs cpol and cpha determine the clock polarity and clock phase of
20 -- the
21 -- transmitted dat. cpol determines whether the clock idles at 0 or 1. cpha
22 -- determines whether the data must be sampled on the leading or trailing
23 -- edge of the shift clock. The values of cpol and cpha are set to be
24 -- compatible with the SPI slave that receives the data.
25
26 -- Outputs: txd, sck, ss_bar
27 -- Output sck is used as the sample clock by the slave.
28
29 -----
30
31 library ieee;
32 use ieee.numeric_std.all;
33 use ieee.std_logic_1164.all;
34 library work;
35 use work.all;
36
37 entity spi_tx_shifter is
38 port(
39     rst_bar : in std_logic;      -- asynchronous system reset
40     clk : in std_logic;          -- system clock
41     send_en : in std_logic;      -- enable data transmission
42     cpha : in std_logic;         -- clock phase
43     cpol : in std_logic;         -- clock polarity
44     data_in : in std_logic_vector(7 downto 0); -- data to send
45     txd : out std_logic;         -- serial output data
46     sck : out std_logic;         -- synchronous shift clock
47     ss_bar : out std_logic       -- slave select
48 );
49
50 end spi_tx_shifter;
51
52 architecture fsm of spi_tx_shifter is

```

```

51
52
53 type state is (idle, ph1, ph2);
54 signal present_state, next_state: state;
55 signal bit_addr : unsigned(2 downto 0);
56
57 begin
58
59
60     state_reg: process(clk, rst_bar)
61     begin
62         -- Present State will be idle when
63         -- reset bar is triggered
64         if rst_bar = '0' then
65             present_state <= idle;
66             -- Present state will change to the
67             -- next state only on the rising
68             -- edge of clock
69         elsif rising_edge(clk) then
70             present_state <= next_state;
71         end if;
72     end process;
73
74     -- Only when send_en is high is when next state goes
75     -- to phase 1, otherwise it goes to phase 2 from idle
76     -- When bit adder is 000, it goes back to idle.
77     nxt_state: process (present_state, send_en, bit_addr)
78     begin
79         case present_state is
80             when idle =>
81                 --
82                 if send_en = '1' then
83                     next_state <= ph1;
84                 else
85                     next_state <= ph2;
86                 end if;
87
88             when ph1 =>
89                 next_state <= ph2;
90
91             when ph2 =>
92                 if bit_addr = "000" then
93                     next_state <= idle;
94                 else
95                     next_state <= ph1;
96                 end if;
97             end case;
98         end process;
99
100     -- Values to be assigned to the output signals
101     -- based on the current state and value of
102     -- bit adder
103     output: process (present_state, data_in, bit_addr)
104     begin
105         case present_state is
106             when idle=>

```




```
108         sck <= cpol;
109         ss_bar <= '1';
110         txd <= data_in(to_integer(bit_addr));
111         when ph1=>
112             sck<=cpol;
113             ss_bar<='0';
114             txd<= data_in(to_integer(bit_addr));
115         when ph2=>
116             sck <= not cpol;
117             ss_bar <= '0';
118             txd <= data_in(to_integer(bit_addr));
119         end case;
120     end process;
121
122     -- Bit counter is used to implement shifting by using count to
123     -- select which bit from the parallel input data is output
124     bit_counter: process (rst_bar, clk, present_state)
125     begin
126         if rst_bar = '0' or present_state = idle then
127             bit_addr <= "111";
128         elsif rising_edge(clk) then
129             if present_state = ph2 then
130                 if bit_addr /= "000" then
131                     bit_addr <= bit_addr - 1;
132                 end if;
133             end if;
134         end if;
135     end process;
136
137
138 end fsm;
```

```

1  -----
2  --
3  -- Title      : task2_tb
4  -- Design     : task1_2
5  -- Author     : Ishabul Haque and Ken Ejinkonye
6  -- Company    : Stony Brook
7  --
8  -- Description : Non-self checking testbench for spi_tx_shifter
9  -----
10
11
12 library ieee;
13 use ieee.std_logic_1164.all;
14 use ieee.numeric_std.all;
15 library work;
16 use work.all;
17
18
19 entity task2_tb is
20     -- Generic declarations of the tested unit
21
22
23
24
25 --}} End of automatically maintained section
26 end task2_tb;
27
28 architecture tb_architecture of task2_tb is
29
30
31     --stimulus signals
32     signal rst_bar : std_logic;
33     signal send : std_logic := '1';
34     signal clk : std_logic := '0';
35     signal cpha: std_logic := '0';
36     signal cpol: std_logic := '0';
37     signal data_in: std_logic_vector(7 downto 0);
38
39     --observed signals
40     signal send_en: std_logic;
41     signal txd: std_logic;
42     signal sck: std_logic;
43     signal ss_bar: std_logic;
44
45
46     constant period : time := 20ns; --need a much longer period
47                                     -- in actual hardware
48
49 begin
50     -- Unit Under Test port map
51     UUT: entity spi_tx_shifter
52     port map (
53         rst_bar => rst_bar,
54         clk => clk,
55         send_en => send_en,

```

```
56         cpha => cpha,
57         cpol => cpol,
58         data_in => data_in,
59         txd => txd,
60         sck => sck,
61         ss_bar => ss_bar
62     );
63
64     -- Port mapping for send_en from send_pos_edge_det
65     -- design to spi_tx_shifter design
66     u0 : entity send_pos_edge_det
67     port map(
68         rst_bar => rst_bar, clk => clk,
69         send_en => send_en,
70         send=>send);
71     rst_bar <= '0', '1' after period * 3;    -- reset
72
73     clock: process                                -- system clock
74     begin
75         -- clock starts at 0 for 0.5 clock periods
76         for i in 0 to 28 loop
77             wait for period;
78             clk <= not clk;                        -- 28 rising edges
79             wait for period;
80         end loop;                                -- stop clock
81         std.env.finish;
82     end process;
83
84
85
86
87 end tb_architecture;
88
```

 

```

1  -----
2  --
3  -- Title      : SPI_test_system
4  -- Design     : task1_2
5  -- Author     : Ishabul Haque and Ken Ejinkonye
6  -- Company    : Stony Brook
7  --
8  -- Description : The top-level structure simply combines the two previous
9  -- entities
10 -- send_pos_edge_det and spi_tx_shifter.
11 -- List of Circuit Features to be verified:
12 -- Inputs: rst_bar, clk, send, cpol, cpha, data_in
13 -- Outputs: mosi, sck, ss_bar
14 -- Observant Stimulus: Present State, Next State
15 -----
16
17 library IEEE;
18 use IEEE.std_logic_1164.all;
19 library work;
20 use work.all;
21
22 entity SPI_test_system_I is
23     port(
24         rst_bar : in std_logic;      -- asynchnronous system reset
25         clk : in std_logic;          -- system clock
26         send : in std_logic;         -- debounced send input
27         cpol : in std_logic;         -- clock poolarity setting
28         cpha : in std_logic;         -- clock phase setting
29         data_in : in std_logic_vector(7 downto 0); -- parallel input data
30         mosi: out std_logic;         -- master out slave in SPI serial data
31         sck: out std_logic;          -- SPI shift clock to slave
32         ss_bar : out std_logic       -- SPI shift clock to slave
33     );
34 end SPI_test_system_I;
35
36 architecture structural of SPI_test_system_I is
37     signal temp_send_en : std_logic;
38
39 begin
40
41
42 -- Port Map for first two designs to structural design SPI_test_system
43 u0 : entity send_pos_edge_det port map(rst_bar => rst_bar, clk => clk,
44     send => send, send_en => temp_send_en);
45
46 u1: entity spi_tx_shifter port map(rst_bar => rst_bar, clk => clk,
47     cpol => cpol, cpha => cpha, data_in => data_in, sck => sck,
48     ss_bar => ss_bar, send_en => temp_send_en, txd => mosi);
49
50
51
52
53 end structural;


```

```

1  -----
2  --
3  -- Title      : task3_tb
4  -- Design     : task1_2
5  -- Author     : Ishabul Haque and Ken Ejinkonye
6  -- Company    : Stony Brook
7  --
8  -- Description : Non self checking test bench for SPI_test_system
9  -----
10
11
12 library ieee;
13 use ieee.std_logic_1164.all;
14 use ieee.numeric_std.all;
15 library work;
16 use work.all;
17
18
19
20 entity task3_tb is
21     -- Generic declarations of the tested unit
22
23
24
25
26 --}} End of automatically maintained section
27 end task3_tb;
28
29 architecture tb_architecture of task3_tb is
30
31
32     --stimulus signals
33     signal rst_bar : std_logic;
34     signal send : std_logic := '1';
35     signal cpha : std_logic;
36     signal cpol: std_logic;
37     signal clk : std_logic := '0';
38
39     signal data_in: std_logic_vector(7 downto 0);
40
41     --observed signals
42     signal send_en: std_logic;
43     signal txd: std_logic;
44     signal sck: std_logic;
45     signal ss_bar: std_logic;
46     signal present_state:std_logic;
47     signal next_state:std_logic;
48     signal mosi : std_logic;
49
50     constant period : time := 20ns; --need a much longer period
51                                     -- in actual hardware
52
53 begin
54     -- Unit Under Test port map
55

```

```
56     u0 : entity send_pos_edge_det port map(rst_bar => rst_bar, clk => clk,
57     send => send, send_en => send_en);
58
59     u1: entity spi_tx_shifter port map(rst_bar => rst_bar, clk => clk,
60     cpol => cpol, cpha => cpha, data_in => data_in, sck => sck,
61     ss_bar => ss_bar, send_en => send_en, txd => mosi);
62
63     rst_bar <= '0', '1' after period * 3;    -- reset
64
65     clock: process                                -- system clock
66     begin
67         -- clock starts at 0 for 0.5 clock periods
68         for i in 0 to 28 loop
69             wait for period;
70             clk <= not clk;    -- 15 rising edges
71             wait for period;
72         end loop;            -- stop clock
73         std.env.finish;
74     end process;
75
76     snd: process
77     begin
78         for i in 0 to 28 loop    --28 rising edges
79             wait for 200ns;    -- Send pulse duration of 200ns
80             send <= not send;
81         end loop;            --end pulse
82
83         std.env.finish;
84     end process;
85
86
87
88 end tb_architecture;
89
```

 

1. How long is the send_en pulse generated by send_pos_edge_det? State this time duration as both number of clock pulses and as ns.
 - a. The send_en pulse generated by the designs task is 80ns long and is the duration of two clock pulses
2. What is the frequency relationship between the SPI clock sck and the system clock clk?
 - a. The frequency of SPI clock sck is half of system clock clk.
3. From the log file determine the default state assignment encoding used by the synthesizer for your FSMs.