

Lab 8: Simple SPI Transmitter

Ishabul Haque 111598085

Ken Ejinkonye 112011486

Section 2

04/10/20

```

1  -----
2  --
3  -- Title       : send_pos_edge_det
4  -- Design      : task1_2
5  -- Author      : Ishabul Haque and Ken Ejinkonye
6  -- Company     : Stony Brook
7  --
8  -- Description : A positive edge detector is used to detect the
9  -- positive edge of the send and to generate a narrow pulse that will
10 -- be used by the spi_tx_shifter to determine when it should start to send
11 -- a byte.
12 -- List of Circuit Features To Be Verified:
13 -- Inputs: rst_bar, clk, send
14 -- Outputs: send_en
15
16
17 -----
18
19 library IEEE;
20 use IEEE.std_logic_1164.all;
21
22 entity send_pos_edge_det is
23     port(
24         rst_bar : in std_logic;    -- asynchnronous system reset
25         clk : in std_logic;        -- system clock
26         send : in std_logic;       -- debounced send input
27         send_en : out std_logic    -- send enable output pulse
28     );
29 end send_pos_edge_det;
30
31
32 architecture moore_fsm of send_pos_edge_det is
33     type state is (state_a, state_b, state_c);
34     signal present_state, next_state : state;
35
36     begin
37         state_reg: process (clk,rst_bar)
38         begin
39             if rst_bar = '0' then
40                 -- If rst_bar is enabled, then present state will switch
41                 -- to state a
42                 present_state <= state_a;
43             elsif rising_edge(clk) then
44                 -- If rst_bar is not enabled, the present state will switch
45                 -- to the next state on the rising edge of clock
46                 present_state <= next_state;
47             end if;
48         end process;
49
50         outputs: process (present_state)
51         begin
52             case present_state is
53                 -- Output send_en will only be high when the present state
54                 -- is in state c, otherwise it will output low
55                 when state_c => send_en <= '1';

```


```
56         when others => send_en <= '0';
57     end case;
58 end process;
59
60     nxt_state: process (present_state, send)
61     begin
62         -- Moore FSM, state values are determined by
63         -- state diagram
64         case present_state is
65             when state_a =>
66                 if send = '0' then
67                     next_state <= state_b;
68                 else
69                     next_state <= state_b;
70                 end if;
71
72             when state_b =>
73                 if send = '1' then
74                     next_state <= state_c;
75                 else
76                     next_state <= state_b;
77                 end if;
78
79             when others =>
80                 if send = '0' then
81                     next_state <= state_b;
82                 else
83                     next_state <= state_a;
84                 end if;
85             end case;
86         end process;
87     end moore_fsm;
88
89
90
```

```

1  -----
2  ---
3  -- Title      : send_pos_edge_det_tb
4  -- Design     : task1_2
5  -- Author     : Ishabul Haque and Ken Ejinkonye
6  -- Company    : Stony Brook
7  --
8  -- Description : Non self checking testbench for send_pos_edge_det design.
9  --
10 -----
11 ---
12
13 library ieee;
14 use ieee.std_logic_1164.all;
15 use ieee.numeric_std.all;
16 library work;
17 use work.all;
18
19
20
21 entity send_pos_edge_det_TB is
22
23
24 end send_pos_edge_det_TB;
25
26 architecture tb_architecture of send_pos_edge_det_TB is
27
28
29     --stimulus signals
30     signal rst_bar : std_logic;
31     signal send : std_logic;
32     signal clk : std_logic;
33     --observed signals
34     signal send_en : std_logic;
35
36     constant period : time := 20ns; --need a much longer period
37                                     -- in actual hardware
38
39 begin
40     -- Unit Under Test port map
41     UUT: entity send_pos_edge_det
42     port map (
43         clk => clk,
44         rst_bar => rst_bar,
45         send => send,
46         send_en => send_en
47     );
48
49     rst_bar <= '0', '1' after period; -- reset
50
51     clock: process -- system clock
52     begin
53         -- clock starts at 0 for 0.5 clock periods
54         for i in 0 to 28 loop
55             wait for period;

```

```
56         clk <= not clk;           -- 28 rising edges
57         wait for period;
58     end loop;                     -- stop clock
59     std.env.finish;
60 end process;
61
62 -- Duration of signal send is 200ns at a high value
63 snd: process
64 begin
65     for i in 0 to 28 loop         --28 rising edges
66         wait for 200ns;           -- Send pulse duration of 200ns
67         send <= not send;
68     end loop;                     --end pulse
69
70     std.env.finish;
71 end process;
72
73 end tb_architecture;
74
```

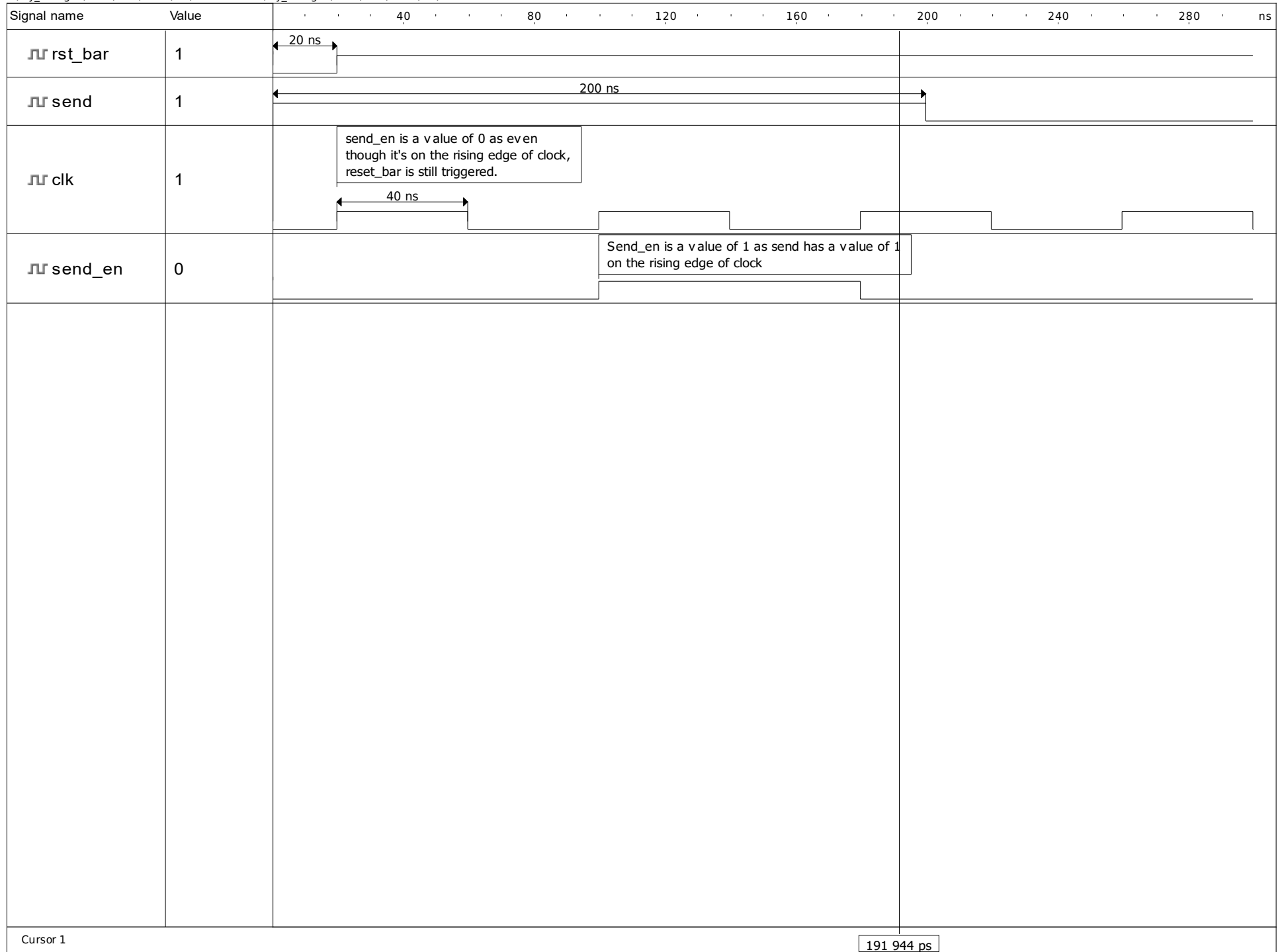

```

1  -----
2  --
3  -- Title      : spi_tx_shifter
4  -- Design     : task1_2
5  -- Author     : Ishabul Haque and Ken Ejinkonye
6  -- Company    : Stony Brook
7  --
8  -- Description : The transmitter shifter spi_tx_shifter converts the
9  parallel
10 -- data byte data_in to serial and transmits its data bits along with a
11 -- synchronous clock sck. An SPI slave uses sck to determine when to
12 -- sample
13 -- each serial data bit. We will be transmitting the data's most
14 -- significant
15 -- bit.
16
17 -- List of Circuit Features To Be Verified:
18 -- Inputs: rst_bar, clk, send_en, cpha, cpol, data_in
19 -- Inputs cpol and cpha determine the clock polarity and clock phase of
20 -- the
21 -- transmitted dat. cpol determines whether the clock idles at 0 or 1. cpha
22 -- determines whether the data must be sampled on the leading or trailing
23 -- edge of the shift clock. The values of cpol and cpha are set to be
24 -- compatible with the SPI slave that receives the data.
25
26 -- Outputs: txd, sck, ss_bar
27 -- Output sck is used as the sample clock by the slave.
28
29 -----
30
31 library ieee;
32 use ieee.numeric_std.all;
33 use ieee.std_logic_1164.all;
34 library work;
35 use work.all;
36
37 entity spi_tx_shifter is
38 port(
39     rst_bar : in std_logic;      -- asynchronous system reset
40     clk : in std_logic;          -- system clock
41     send_en : in std_logic;      -- enable data transmission
42     cpha : in std_logic;         -- clock phase
43     cpol : in std_logic;         -- clock polarity
44     data_in : in std_logic_vector(7 downto 0); -- data to send
45     txd : out std_logic;         -- serial output data
46     sck : out std_logic;         -- synchronous shift clock
47     ss_bar : out std_logic       -- slave select
48 );
49
50 end spi_tx_shifter;
51
52 architecture fsm of spi_tx_shifter is

```

```

51
52
53 type state is (idle, ph1, ph2);
54 signal present_state, next_state: state;
55 signal bit_addr : unsigned(2 downto 0);
56
57 begin
58
59
60     state_reg: process(clk, rst_bar)
61     begin
62         -- Present State will be idle when
63         -- reset bar is triggered
64         if rst_bar = '0' then
65             present_state <= idle;
66             -- Present state will change to the
67             -- next state only on the rising
68             -- edge of clock
69         elsif rising_edge(clk) then
70             present_state <= next_state;
71         end if;
72     end process;
73
74     -- Only when send_en is high is when next state goes
75     -- to phase 1, otherwise it goes to phase 2 from idle
76     -- When bit adder is 000, it goes back to idle.
77     nxt_state: process (present_state, send_en, bit_addr)
78     begin
79         case present_state is
80             when idle =>
81                 --
82                 if send_en = '1' then
83                     next_state <= ph1;
84                 else
85                     next_state <= ph2;
86                 end if;
87
88             when ph1 =>
89                 next_state <= ph2;
90
91             when ph2 =>
92                 if bit_addr = "000" then
93                     next_state <= idle;
94                 else
95                     next_state <= ph1;
96                 end if;
97             end case;
98         end process;
99
100     -- Values to be assigned to the output signals
101     -- based on the current state and value of
102     -- bit adder
103     output: process (present_state, data_in, bit_addr)
104     begin
105         case present_state is
106             when idle=>

```




```
108         sck <= cpol;
109         ss_bar <= '1';
110         txd <= data_in(to_integer(bit_addr));
111         when ph1=>
112             sck<=cpol;
113             ss_bar<='0';
114             txd<= data_in(to_integer(bit_addr));
115         when ph2=>
116             sck <= not cpol;
117             ss_bar <= '0';
118             txd <= data_in(to_integer(bit_addr));
119         end case;
120     end process;
121
122     -- Bit counter is used to implement shifting by using count to
123     -- select which bit from the parallel input data is output
124     bit_counter: process (rst_bar, clk, present_state)
125     begin
126         if rst_bar = '0' or present_state = idle then
127             bit_addr <= "111";
128         elsif rising_edge(clk) then
129             if present_state = ph2 then
130                 if bit_addr /= "000" then
131                     bit_addr <= bit_addr - 1;
132                 end if;
133             end if;
134         end if;
135     end process;
136
137
138 end fsm;
```

```

1  -----
2  --
3  -- Title      : task2_tb
4  -- Design     : task1_2
5  -- Author     : Ishabul Haque and Ken Ejinkonye
6  -- Company    : Stony Brook
7  --
8  -- Description : Non-self checking testbench for spi_tx_shifter
9  -----
10
11
12 library ieee;
13 use ieee.std_logic_1164.all;
14 use ieee.numeric_std.all;
15 library work;
16 use work.all;
17
18
19 entity task2_tb is
20     -- Generic declarations of the tested unit
21
22
23
24
25 --}} End of automatically maintained section
26 end task2_tb;
27
28 architecture tb_architecture of task2_tb is
29
30
31     --stimulus signals
32     signal rst_bar : std_logic;
33     signal send : std_logic := '1';
34     signal clk : std_logic := '0';
35     signal cpha: std_logic := '0';
36     signal cpol: std_logic := '0';
37     signal data_in: std_logic_vector(7 downto 0);
38
39     --observed signals
40     signal send_en: std_logic;
41     signal txd: std_logic;
42     signal sck: std_logic;
43     signal ss_bar: std_logic;
44
45
46     constant period : time := 20ns; --need a much longer period
47                                     -- in actual hardware
48
49 begin
50     -- Unit Under Test port map
51     UUT: entity spi_tx_shifter
52     port map (
53         rst_bar => rst_bar,
54         clk => clk,
55         send_en => send_en,

```

```
56         cpha => cpha,
57         cpol => cpol,
58         data_in => data_in,
59         txd => txd,
60         sck => sck,
61         ss_bar => ss_bar
62     );
63
64     -- Port mapping for send_en from send_pos_edge_det
65     -- design to spi_tx_shifter design
66     u0 : entity send_pos_edge_det
67     port map(
68         rst_bar => rst_bar, clk => clk,
69         send_en => send_en,
70         send=>send);
71     rst_bar <= '0', '1' after period * 3;    -- reset
72
73     clock: process                                -- system clock
74     begin
75         -- clock starts at 0 for 0.5 clock periods
76         for i in 0 to 28 loop
77             wait for period;
78             clk <= not clk;                        -- 28 rising edges
79             wait for period;
80         end loop;                                -- stop clock
81         std.env.finish;
82     end process;
83
84
85
86
87 end tb_architecture;
88
```

 

```

1  -----
2  --
3  -- Title       : SPI_test_system
4  -- Design      : task1_2
5  -- Author      : Ishabul Haque and Ken Ejinkonye
6  -- Company     : Stony Brook
7  --
8  -- Description : The top-level structure simply combines the two previous
9  -- entities
10 -- send_pos_edge_det and spi_tx_shifter.
11 -- List of Circuit Features to be verified:
12 -- Inputs: rst_bar, clk, send, cpol, cpha, data_in
13 -- Outputs: mosi, sck, ss_bar
14 -- Observant Stimulus: Present State, Next State
15 -----
16
17 library IEEE;
18 use IEEE.std_logic_1164.all;
19 library work;
20 use work.all;
21
22 entity SPI_test_system_I is
23     port(
24         rst_bar : in std_logic;      -- asynnnchronous system reset
25         clk : in std_logic;          -- system clock
26         send : in std_logic;         -- debounced send input
27         cpol : in std_logic;         -- clock poolarity setting
28         cpha : in std_logic;         -- clock phase setting
29         data_in : in std_logic_vector(7 downto 0); -- parallel input data
30         mosi: out std_logic;         -- master out slave in SPI serial data
31         sck: out std_logic;          -- SPI shift clock to slave
32         ss_bar : out std_logic       -- SPI shift clock to slave
33     );
34 end SPI_test_system_I;
35
36 architecture structural of SPI_test_system_I is
37     signal temp_send_en : std_logic;
38
39 begin
40
41
42 -- Port Map for first two designs to structural design SPI_test_system
43 u0 : entity send_pos_edge_det port map(rst_bar => rst_bar, clk => clk,
44     send => send, send_en => temp_send_en);
45
46 u1: entity spi_tx_shifter port map(rst_bar => rst_bar, clk => clk,
47     cpol => cpol, cpha => cpha, data_in => data_in, sck => sck,
48     ss_bar => ss_bar, send_en => temp_send_en, txd => mosi);
49
50
51
52
53 end structural;

```

```
1  -----
2  --
3  -- Title      : task3_tb
4  -- Design     : task1_2
5  -- Author     : Ishabul Haque and Ken Ejinkonye
6  -- Company    : Stony Brook
7  --
8  -- Description : Non self checking test bench for SPI_test_system
9  -----
10
11
12 library ieee;
13 use ieee.std_logic_1164.all;
14 use ieee.numeric_std.all;
15 library work;
16 use work.all;
17
18
19
20 entity task3_tb is
21     -- Generic declarations of the tested unit
22
23
24
25
26 --}} End of automatically maintained section
27 end task3_tb;
28
29 architecture tb_architecture of task3_tb is
30
31
32     --stimulus signals
33     signal rst_bar : std_logic;
34     signal send : std_logic := '1';
35     signal cpha : std_logic;
36     signal cpol: std_logic;
37     signal clk : std_logic := '0';
38
39     signal data_in: std_logic_vector(7 downto 0);
40
41     --observed signals
42     signal send_en: std_logic;
43     signal txd: std_logic;
44     signal sck: std_logic;
45     signal ss_bar: std_logic;
46     signal present_state:std_logic;
47     signal next_state:std_logic;
48     signal mosi : std_logic;
49
50     constant period : time := 20ns; --need a much longer period
51                                     -- in actual hardware
52
53 begin
54     -- Unit Under Test port map
55
```

```
56     u0 : entity send_pos_edge_det port map(rst_bar => rst_bar, clk => clk,
57     send => send, send_en => send_en);
58
59     u1: entity spi_tx_shifter port map(rst_bar => rst_bar, clk => clk,
60     cpol => cpol, cpha => cpha, data_in => data_in, sck => sck,
61     ss_bar => ss_bar, send_en => send_en, txd => mosi);
62
63     rst_bar <= '0', '1' after period * 3;    -- reset
64
65     clock: process                                -- system clock
66     begin
67         -- clock starts at 0 for 0.5 clock periods
68         for i in 0 to 28 loop
69             wait for period;
70             clk <= not clk;    -- 15 rising edges
71             wait for period;
72         end loop;            -- stop clock
73         std.env.finish;
74     end process;
75
76     snd: process
77     begin
78         for i in 0 to 28 loop    --28 rising edges
79             wait for 200ns;    -- Send pulse duration of 200ns
80             send <= not send;
81         end loop;            --end pulse
82
83         std.env.finish;
84     end process;
85
86
87
88 end tb_architecture;
89
```

